

Figure 2. Graphical Attenuation Calculation for a Shunt Capacitor.

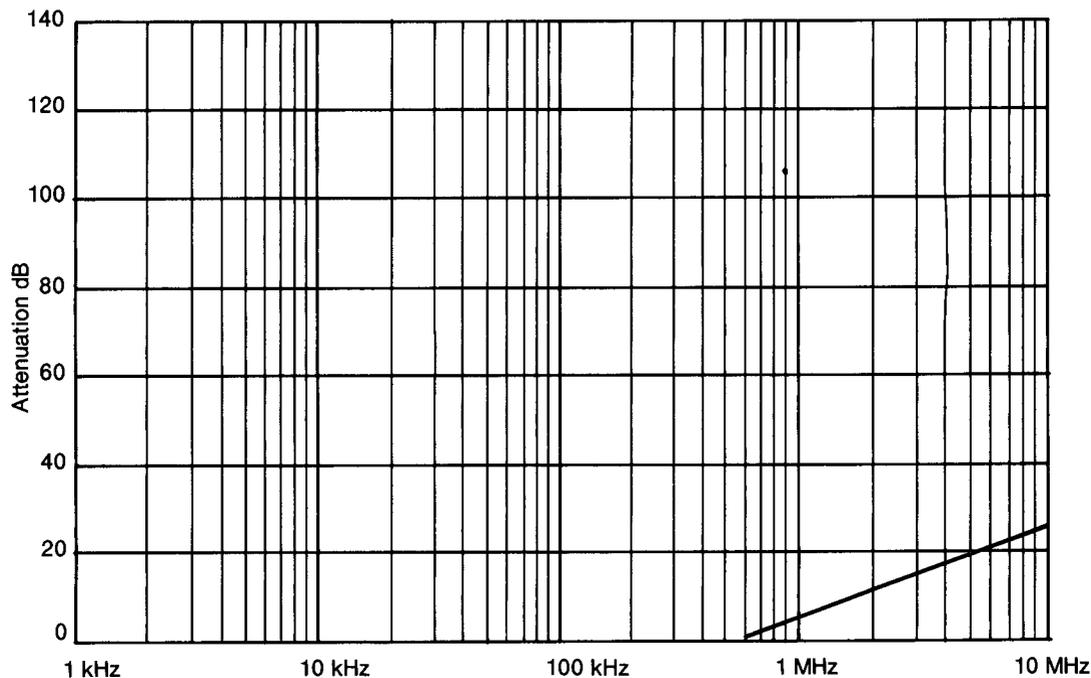


Figure 3. Plot of Attenuation for a 0.01 μF Capacitor in a 50 Ω System.

impedance, Z_l , $Z_{\text{sum}} = Z_s + Z_l$, $Z_p = Z_s/Z_l$. For a low pass filter, the shunt element of a filter is presumed to be a capacitor with an impedance of Z_{cap} . The series element is presumed to be an inductor, with an impedance of Z_{ind} .

By plotting the reference impedance and the filter element impedance, the impedance mismatch (and hence attenuation) can be read directly from the graph paper. A more rigorous explanation is possible by considering the expression² for attenuation for a shunt element filter.

$$A = 20 \text{Log}_{10} [1 + Z_p/Z_{\text{cap}}] = 20 \text{Log}_{10} [Z_p + Z_{\text{cap}}/Z_{\text{cap}}] \quad (1)$$

$$A = 20 \text{Log}_{10} [Z_p + Z_{\text{cap}}] - 20 \text{Log}_{10} [Z_{\text{cap}}] \quad (2)$$

Careful consideration of the above expression will reveal that as Z_{cap} becomes smaller, the attenuation increases. Also, as Z_{cap} becomes larger, the expression for attenuation approaches 0 dB. If an additional limitation is imposed, that the expression will only be valid for $Z_{\text{cap}} < Z_p$, an additional simplification may be made:

$$A = 20 \text{Log}_{10} [1 + Z_p/Z_{\text{cap}}] \approx 20 \text{Log}_{10} [Z_p/Z_{\text{cap}}] \quad (3)$$

which may be expressed as

$$A = 20 \text{Log}_{10} [Z_p] - 20 \text{Log}_{10} [Z_{\text{cap}}] \quad (4)$$

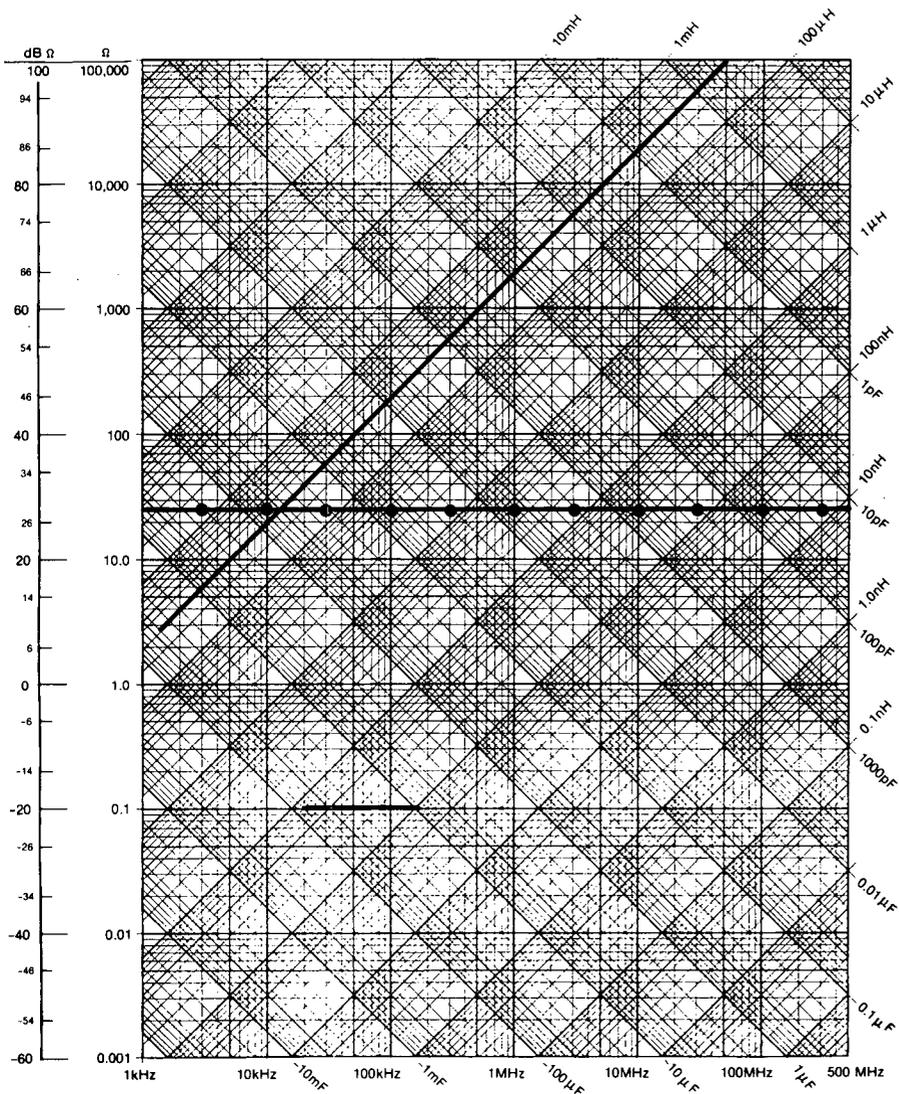


Figure 4. Graphical Solution to Common Mode Choke Attenuation.

Above is the expression which allows direct use of the graphical attenuation method for a shunt capacitor.

A similar derivation for the expression of attenuation of a series inductor gives the result that

$$A = 20 \text{ Log}_{10} [Z_{\text{ind}}] - 20 \text{ Log}_{10} [Z_{\text{sum}}] \quad (5)$$

Again, for a series inductor, attenuation only occurs when Z_{ind} is greater than the reference impedance, Z_{sum} .

GRAPHICAL ATTENUATION FOR A SINGLE ELEMENT CAPACITIVE FILTER

Using impedance paper, one may employ the following method to estimate attenuation versus frequency.

1. Plot the source and load impedance on impedance paper (Z -paper).
2. Use a dotted line to mark the parallel combination (Z_p) of the source and load impedance.
3. Plot the impedance of the filter capacitor, (Z_{cap}), versus frequency.
4. The attenuation region due for shunt filter (Z_{cap}) is the region in which the filter impedance (Z_{cap}) is less than Z_p . The attenuation is approximately $20 \text{ Log} [Z_p/Z_{\text{cap}}]$ in this region.

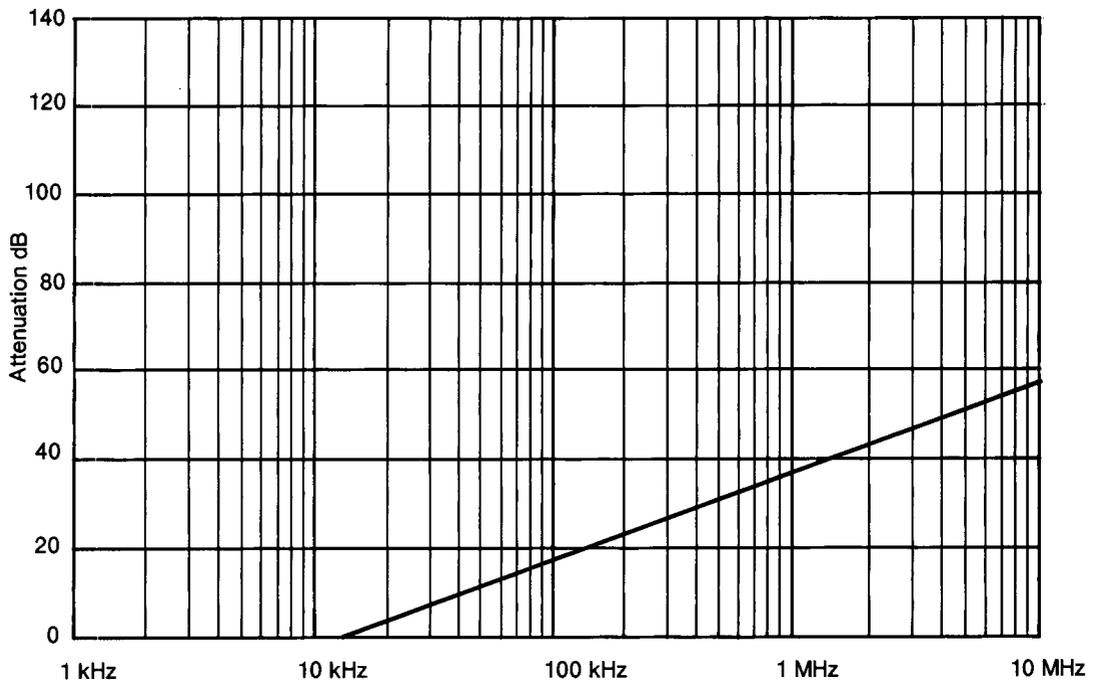


Figure 5. Plot of Attenuation for a Common Mode Choke.

Example Problem 1: Attenuation of a Shunt Capacitor in a 50 Ω System

An oscilloscope has a 50 Ω input. A 50 Ω coaxial cable is connected to the oscilloscope and to a homemade probe which has 0.01 μF shunt capacitance. The probe is used to monitor the output of a signal generator (50 Ω output impedance).

1. Calculate the attenuation due to the capacitance of the scope probe at 10 kHz and 10 MHz.
2. Calculate the attenuation at 10 MHz if the capacitance is 0.1 μF .

Solution:

(Part 1)

It is known that the attenuation for a shunt filter is

$$A_{\text{dB}} = 20 \text{ Log} [1 + Z_g/Z_l/Z_{\text{cap}}] \approx 20 \text{ Log} [Z_p/Z_{\text{cap}}] \quad (3-1)$$

First mark Z_p (25 Ω) on the impedance paper then mark $Z_{\text{cap}} = (0.01 \mu\text{F})$ on the impedance paper. Reading off values of Z_{cap} , one finds

| Frequency | Impedance | Attenuation |
|-----------|-----------------------|--|
| 10 kHz | $\approx 1700 \Omega$ | $20 \text{ Log} \left[\frac{1+25}{1700} \right] \approx 0$ |
| 10 MHz | $\approx 1.8 \Omega$ | $20 \text{ Log} \left[\frac{25}{1.8} \right] \approx 23 \text{ dB}$ |

Likewise, one can read off the impedance (in $\text{dB}\Omega$) of Z_{cap} and Z_p (also in $\text{dB}\Omega$) from the Z-paper directly and can subtract impedances to find the attenuation (Figure 2). This approach follows equation (4).

(Part 2)

From the Z-paper, the impedance of 0.1 μF at 10 MHz is $\approx 0.2 \Omega$, or $-14 \text{ dB}\Omega$. Z_p is $28 \text{ dB}\Omega$. The attenuation is then $28 - (-14) = 44 \text{ dB}$. An exact solution is

$$A_{\text{dB}} = 20 \text{ Log} [1 + 20/0.18] = 43 \text{ dB}$$

A plot of the attenuation of the capacitor is shown in Figure 3.

GRAPHICAL ATTENUATION FOR A SINGLE ELEMENT INDUCTIVE FILTER

On impedance paper, one may use the following procedure to calcu-

late the attenuation for a series inductor.

1. Plot the source and load impedance on Z-paper.
2. Using a dotted line, mark the sum of Z_g and Z_l (Z_{sum}).
3. Plot the inductive impedance versus frequency Z_{ind} .
4. The attenuation region due to the inductor, Z_{ind} , is the region in which Z_{ind} is greater than Z_{sum} . The attenuation is $20 \text{ Log} [Z_{\text{ind}}] - 20 \text{ Log} [Z_{\text{sum}}]$ in this region.

Example Problem 2: Attenuation of a Common Mode Choke

The common mode source impedance of a supply is determined to be 0.1 Ω at 100 kHz. The common mode impedance of the LISNs is 25 Ω . A 300 μH common mode choke is to be used as a filter. Calculate the attenuation at 100 kHz.

Solution:

The method for inductors is applied:

1. First plot the source and load impedance on Z-paper.
2. The reference impedance, Z_{sum} , is marked with a dotted line.
3. Plot the impedance of the 300 μH choke.
4. The attenuation at 100 kHz is

$$A_{\text{dB}} = 20 \text{ Log} [200 \Omega] - 20 \text{ Log} [25 \Omega] = 46 \text{ dB}\Omega - 28 \text{ dB}\Omega = 18 \text{ dB}$$

The graphical solution is shown in Figure 4. A plot of attenuation versus frequency is shown in Figure 5.

GRAPHICAL ATTENUATION CALCULATIONS FOR MULTIPLE ELEMENT FILTERS

The Sequential Element Theorem results in a very slight modification of the technique. After using the sequential element theorem, the attenuation of each element is calculated separately. All of the individual attenuations are added together for the total attenuation.

SOLVING FOR ATTENUATION WITH PARASITICS USING THE GRAPHICAL ATTENUATION METHODOLOGY

One of the strengths of the Graphical Attenuation Calculation Methodology is the ease in which the effects of parasitics, the variation of permeability with frequency, and other non-idealities may be handled. The most common parasitics of interest are capacitor lead inductance and inductor parasitic capacitance. The key to accounting for parasitics is simply to modify the magnitude of the impedance of the filtering element to reflect the parasitics. Consider a 300 μH inductor with a shunt resistance of 100 pF . The impedance of the 300 μH choke will increase to roughly 2 $\text{k}\Omega$ before the 100 pF shunt capacitance begins to short out the inductor. As the net impedance becomes capacitive and decreases with increasing frequency, the attenuation is reduced accordingly. ■

REFERENCES

1. EMC Services Seminar notebook on "Filter Design for SMPS."
2. EMC Services, Inc., "Graphical Attenuation Calculations with Applications to Power Line Filters and Digital Interfaces."